

For a 75-kVA, 60-Hz, 4600/240 V distribution transformer whose resistances and leakage reactances are (in ohms):

$$R_1 = 0.846, R_2 = 0.00261, X_1 = 26.8, X_2 = 0.0745, R_c = 220000, X_m = 112000$$

Write a computer program to perform the following:

For LV side operating at 240 V:

- Plot the HV side terminal voltage as a function of the power factor angle at full-load as the load power factor varies from 0.6 pf leading through unity pf to 0.6 pf lagging.
- Plot the efficiency and regulation for the same pf range at full-load, half-load and quarter-load conditions.

If the HV transformer tapings is limited to  $\pm 5\%$ , comment on the results above.